
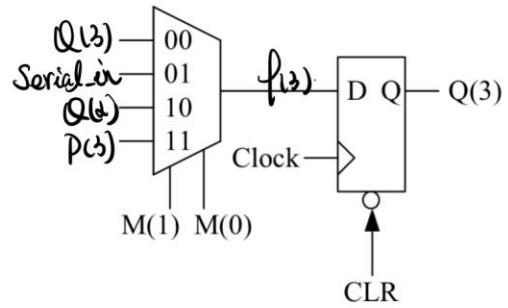
 
 


EE 115B, Fall 2021

Student Name: 朱宇轩 2020531016

Lab 3

1 Schematic (20 points.)

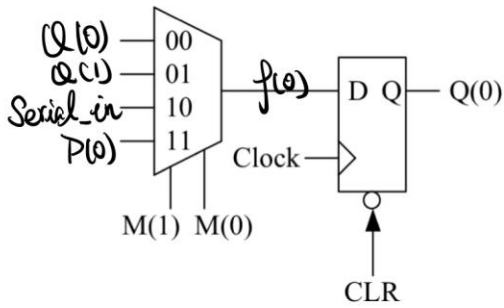

2 Code for Components (10 points. 5 points each.)

2.1 D flip flop

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Dflipflop is
    Port ( D : in STD_LOGIC;
          clr : in STD_LOGIC;
          clock : in STD_LOGIC;
          Q : buffer STD_LOGIC);
end Dflipflop;

architecture Behavioral of Dflipflop is

begin
    process (clr ,clock )
    begin
        if clr = '0' then
            Q <= '0';
        elsif clock'Event and clock = '1' then
            Q <= D;
        end if ;
    end process ;
end Behavioral;
```

2.2 mux4to1

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity mux4to1 is
    Port ( w0 : in STD_LOGIC;
          w1 : in STD_LOGIC;
          w2 : in STD_LOGIC;
          w3 : in STD_LOGIC;
          M : in STD_LOGIC_VECTOR (1 downto 0);
          f : buffer STD_LOGIC);
end mux4to1;

architecture Behavioral of mux4to1 is

begin
    with M select
        f <= w0 when "00",
            w1 when "01",
            w2 when "10",
            w3 when others;
end Behavioral;
```

3 Code for Register (30 points.)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity shiftreg is
    Port ( P : IN std_logic_vector(3 downto 0);
          Q : buffer std_logic_vector(3 downto 0);
          clock : IN std_logic;
          clr : IN std_logic;
          serial_in : IN std_logic;
          M : IN std_logic_vector(1 downto 0)
        );
end shiftreg;
```

```
architecture Structure of shiftreg is
    signal f : std_logic_vector (3 downto 0 );
```

```
component mux4to1
    port ( w0 : in STD_LOGIC;
          w1 : in STD_LOGIC;
          w2 : in STD_LOGIC;
          w3 : in STD_LOGIC;
          M : in STD_LOGIC_VECTOR (1 downto 0);
          f : buffer STD_LOGIC);
end component ;
```

```
component Dflipflop
    port ( D : in STD_LOGIC;
          clr : in STD_LOGIC;
```

```

        clock : in STD_LOGIC;

        Q : buffer STD_LOGIC);

end component ;

begin

mux0: mux4to1 port map
    (Q(0),Q(1),serial_in ,P(0),M(1 downto 0),f(0));

mux1: mux4to1 port map
    (Q(1),Q(2),Q(0),P(1),M(1 downto 0),f(1));

mux2: mux4to1 port map
    (Q(2),Q(3),Q(1) ,P(2),M(1 downto 0),f(2));

mux3: mux4to1 port map
    (Q(3),serial_in ,Q(2),P(3),M(1 downto 0),f(3));


D0: Dflipflop port map
    (f(0),clr ,clock ,Q(0));

D1: Dflipflop port map
    (f(1),clr ,clock ,Q(1));

D2: Dflipflop port map
    (f(2),clr ,clock ,Q(2));

D3: Dflipflop port map
    (f(3),clr ,clock ,Q(3));

end Structure;

```

4 Code for Testbench (20 points.)

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

ENTITY shiftreg_test IS
END shiftreg_test;

ARCHITECTURE behavior OF shiftreg_test IS
-- Component Declaration for the Unit Under Test (UUT)
COMPONENT shiftreg
    PORT(
        P : IN std_logic_vector(3 downto 0);
        Q : buffer std_logic_vector(3 downto 0);
        clock : IN std_logic;
        clr : IN std_logic;
        serial_in : IN std_logic;
        m : IN std_logic_vector(1 downto 0)
    );
END COMPONENT;

--Inputs
signal P : std_logic_vector(3 downto 0) := (others => '0');
signal clock : std_logic := '0';
signal clr : std_logic := '0';
signal serial_in : std_logic := '0';
signal m : std_logic_vector(1 downto 0) := (others => '0');

--Outputs
signal Q : std_logic_vector(3 downto 0);
```

```

-- Clock period definitions
constant clock_period : time := 20ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: shiftreg PORT MAP (
        P => P,
        Q => Q,
        clock => clock,
        clr => clr,
        serial_in => serial_in,
        m => m
    );

-- Clock process definitions
clock_process :process
begin
    clock <= '0';
    wait for clock_period/2;
    clock <= '1';
    wait for clock_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- test CLR
    clr<='0';
    wait for 30ns;

```

```

-- test parallel load

clr<='1';
m<="11";
P<="0110";
wait for 40ns;

-- test right shift

m<="01";
serial_in<='1';
wait for 80ns; -- shift 4 bits

-- test left shift

m<="10";
serial_in <='0';
wait for 80ns; -- shift 4 bits

-- test no change

m<="00";
wait for 10ns;
serial_in <='1';
P<="1111";
wait for 80ns;
wait;

end process;


END;

```


5 Timing Diagram (20 points.)


0-30ns: test CLR

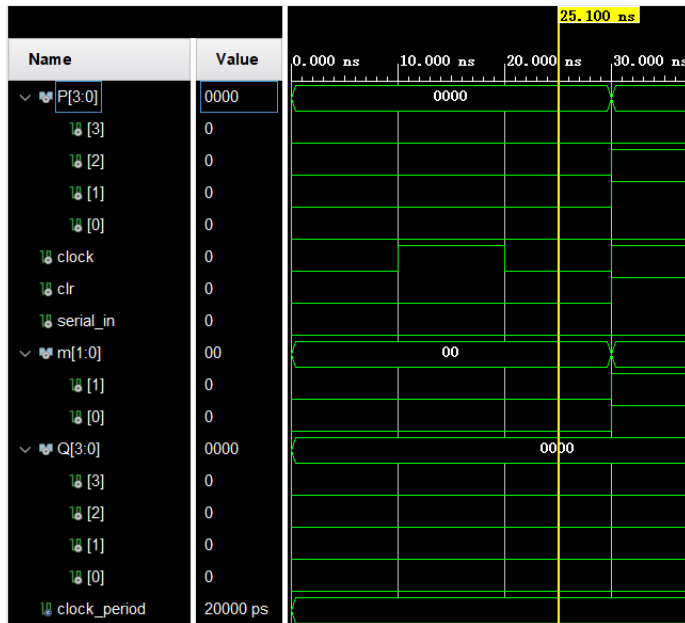All the outputs (Q(3:0)) maintains the value of 0 when clr=0.




30-70ns: test parallel load

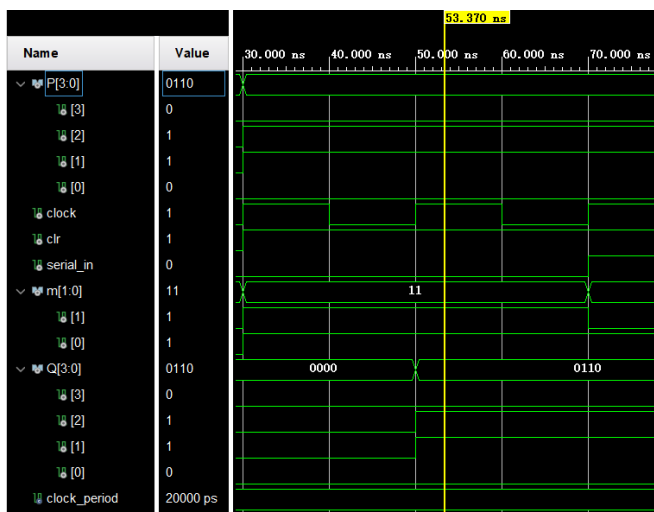After the inputs have been set to the expected value, which is P(3:0)="0110", and waiting for a rising edge of the clock, the outputs turn into Q(3:0)=P(3:0)="0110", which verify the function of parallel load.




70-150ns: test right shift

 Each rising edge of the clock makes all the data shifts to its right bit. And for Q(3), it uses the value of serial_in, which always equal to 1. Moreover, the last rising edge happens at 150ns, thus the 4th shift result is shown in 150-170ns. Then from the simulation, we can see that the value of Q(3:0) changes as we expected, thus we verify the function of right shift.



150-230ns: test left shift

 Each rising edge of the clock makes all the data shifts to its left bit. And for Q(0), it uses the value of serial_in, which always equal to 0. Moreover, the last rising edge happens at 230ns, thus the 4th shift result is shown in 230-250ns. Then from the simulation, we can see that the value of Q(3:0) changes as we expected, thus we verify the function of left shift.



230-∞ ns: test no change

After setting M(1:0)="00", we change the value of P(3:0) and serial_in for example, and we can see the value of Q(3:0) hold its original value at 230ns, thus we verify the function of no change.

